

Application Note

DA9217/DA9220 PCB Layout Recommendations

AN-PM-115

Abstract

This application note provides recommendations on how to place and route the DA9217 or DA9220 device. It also gives guidance on the passive components needed for proper functioning of the system. This document is a guideline only; target applications may have different requirements.

DA9217/DA9220 PCB Layout Recommendations

Contents

Abstract 1

Contents 2

Figures..... 2

1 Terms and Definitions..... 3

2 References 3

3 Introduction..... 4

4 Layout Recommendations 6

 4.1 DA9217 and DA9220 Package Information 6

 4.1.1 DA9217 and DA9220 Ball Map..... 6

 4.1.2 Package Information 7

 4.2 Buck Converter 8

 4.2.1 DA9217 and DA9220 Input..... 8

 4.2.2 Ground Connections 9

 4.2.3 LX Routing 10

 4.2.4 Buck Output 12

 4.2.5 Feedback Lines 12

 4.3 Communication Interface (I²C)..... 14

 4.4 GPIO Signals 14

Revision History 15

Figures

Figure 1: DA9217 Recommended Components and Connections 4

Figure 2: DA9220 Recommended Components and Connections 5

Figure 3: DA9217 and DA9220 Ball Map 6

Figure 4: DA9217 and DA9220 WLCSP Package Outline Drawing 7

Figure 5: Recommended Input Capacitor Placement and Routing 8

Figure 6: Recommended Grounds Connection for DA9220 9

Figure 7: Recommended Grounds Connection for DA9217 10

Figure 8: LX Node Pattern on DA9220 Evaluation Board 11

Figure 9: Output Voltage Feedback Line Routing on DA9220 Evaluation Board 13

Tables

Table 1: DA9217 Recommended Components..... 4

Table 2: DA9220 Recommended Components..... 5

1 Terms and Definitions

FET	Field effect transistor
GND	Ground
GPIO	General purpose input or output
IC	Integrated circuit
PCB	Printed circuit board
WLCSP	Wafer level chip scale packaging

2 References

- [1] DA9217, Datasheet, Dialog Semiconductor.
- [2] DA9220, Datasheet, Dialog Semiconductor.
- [3] AN-PM-010, PCB Layout Guidelines for Dialog PMICs, Application Note, Dialog Semiconductor.

DA9217/DA9220 PCB Layout Recommendations

3 Introduction

Dialog Semiconductor's DA9217 and DA9220 devices are power management ICs with integrated power FETs, see the DA9217 and DA9220 Datasheets [1][2]. DA9217 is configured as a single channel, dual-phase buck converter capable of delivering up to 6 A output current, while DA9220 is configured as a two-channel, single-phase buck converter capable of delivering up to 3 A output current per channel.

The input voltage range of 2.5 V to 5.5 V makes both DA9217 and DA9220 suitable for a wide variety of low-voltage systems including 1S Li-Ion battery-supplied applications. The output voltage is configurable in the range of 0.3 V to 1.9 V.

The recommended components and connections for DA9217 are shown in Figure 1. DA9220's recommended components and connections are shown in Figure 2.

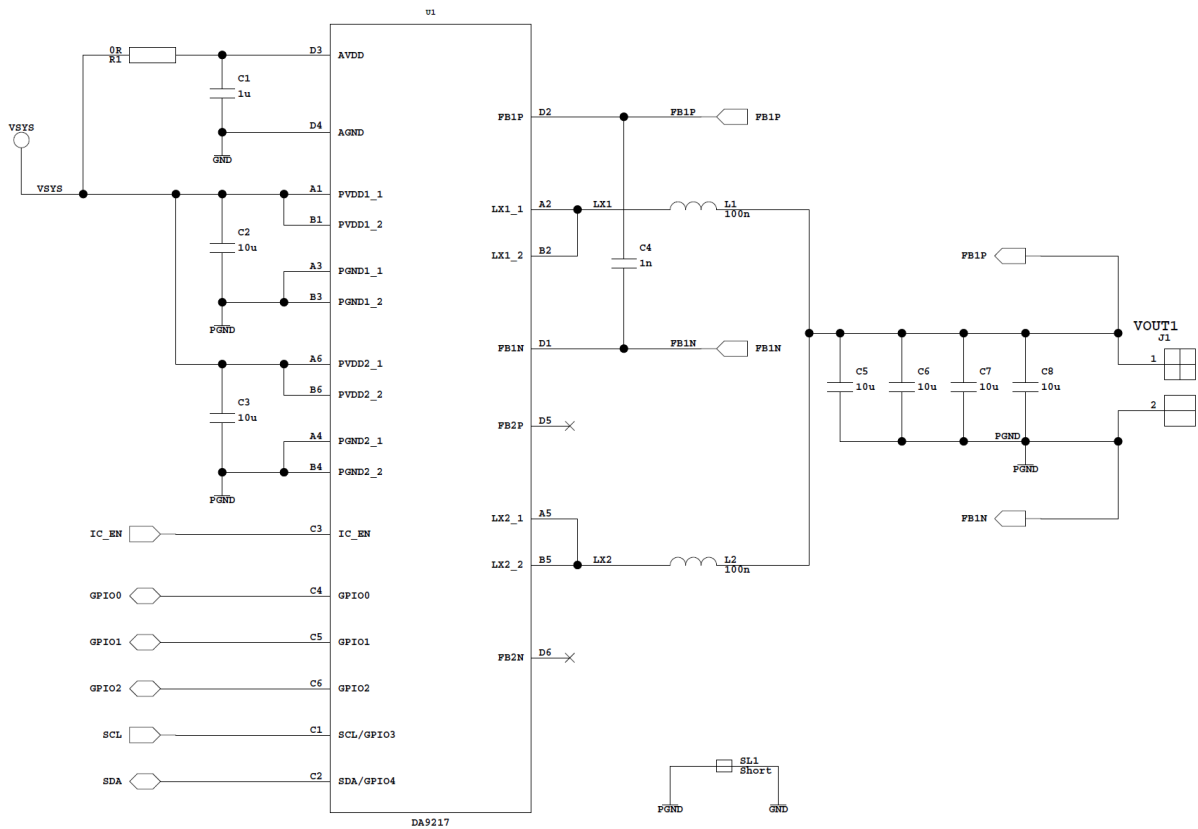


Figure 1: DA9217 Recommended Components and Connections

Table 1: DA9217 Recommended Components

Application	Part Reference	Value	Temp. Char.	Voltage Rating	ISAT and ITEMP
AVDD Bypass Cap	C1	1 µF	X5R or better	16 V or above	N/A
PVDD Bypass Cap	C2, C3	10 µF	X5R or better	16 V or above	N/A
VOUT Bypass Cap	C5, C6, C7, C8	10 µF	X5R or better	6.3 V or above	N/A
FB Bypass Cap	C4	1 nF	X5R or better	6.3 V or above	N/A
Output Inductor	L1, L2	100 nH	N/A	N/A	4A or above

DA9217/DA9220 PCB Layout Recommendations

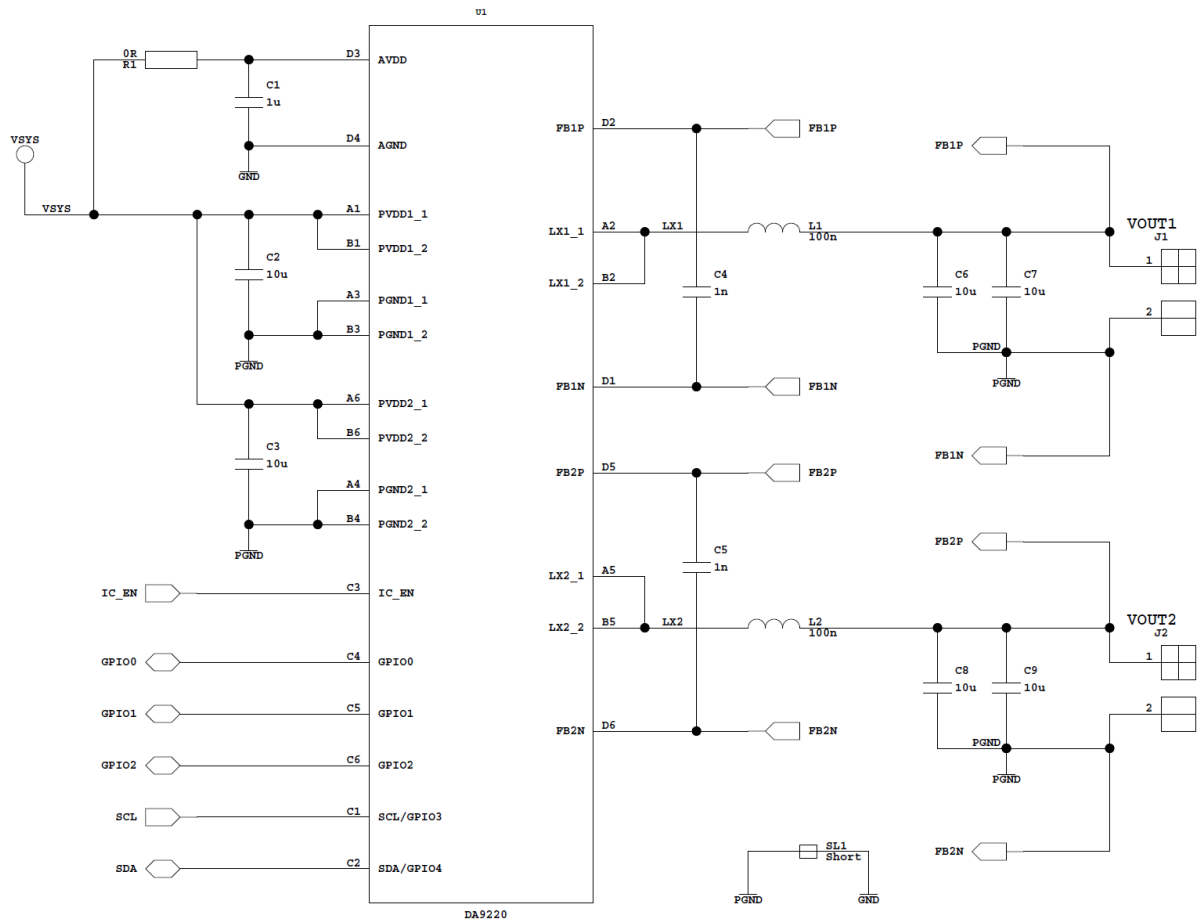


Figure 2: DA9220 Recommended Components and Connections

Table 2: DA9220 Recommended Components

Application	Part Reference	Value	Temp. Char.	Voltage Rating	ISAT and ITEMP
AVDD Bypass Cap	C1	1 µF	X5R or better	16 V or above	N/A
PVDD Bypass Cap	C2, C3	10 µF	X5R or better	16 V or above	N/A
VOUT Bypass Cap	C6, C7, C8, C9	10 µF	X5R or better	6.3 V or above	N/A
FB Bypass Cap	C4, C5	1 nF	X5R or better	6.3 V or above	N/A
Output Inductor	L1, L2	100 nH	N/A	N/A	4 A or above

DA9217/DA9220 PCB Layout Recommendations

4 Layout Recommendations

DA9217 and DA9220 are packaged in a 24-pin WLCSP package with a 0.4 mm pitch.

At least a four-layer PCB stack-up should be used for best PCB layout design. However, the number of routing layers and other PCB parameters are also determined by the other devices in the system.

These recommendations are with reference to the Dialog DA9217/DA9220 Evaluation Board, a six-layer PCB. General PMIC layout guidelines are provided in AN-PM-010 [3].

4.1 DA9217 and DA9220 Package Information

4.1.1 DA9217 and DA9220 Ball Map

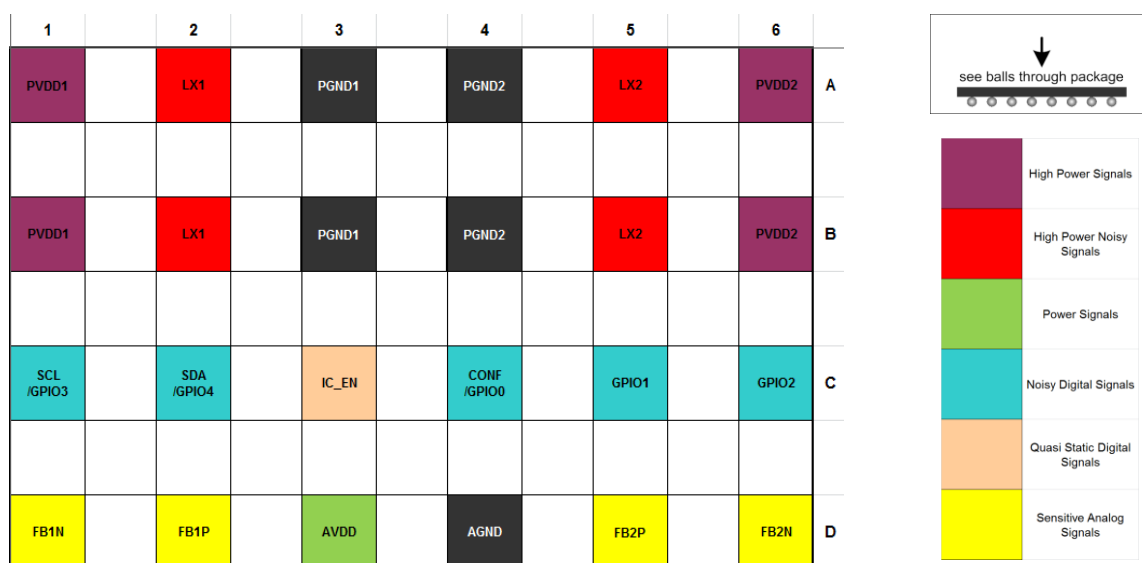


Figure 3: DA9217 and DA9220 Ball Map

DA9217/DA9220 PCB Layout Recommendations

4.1.2 Package Information

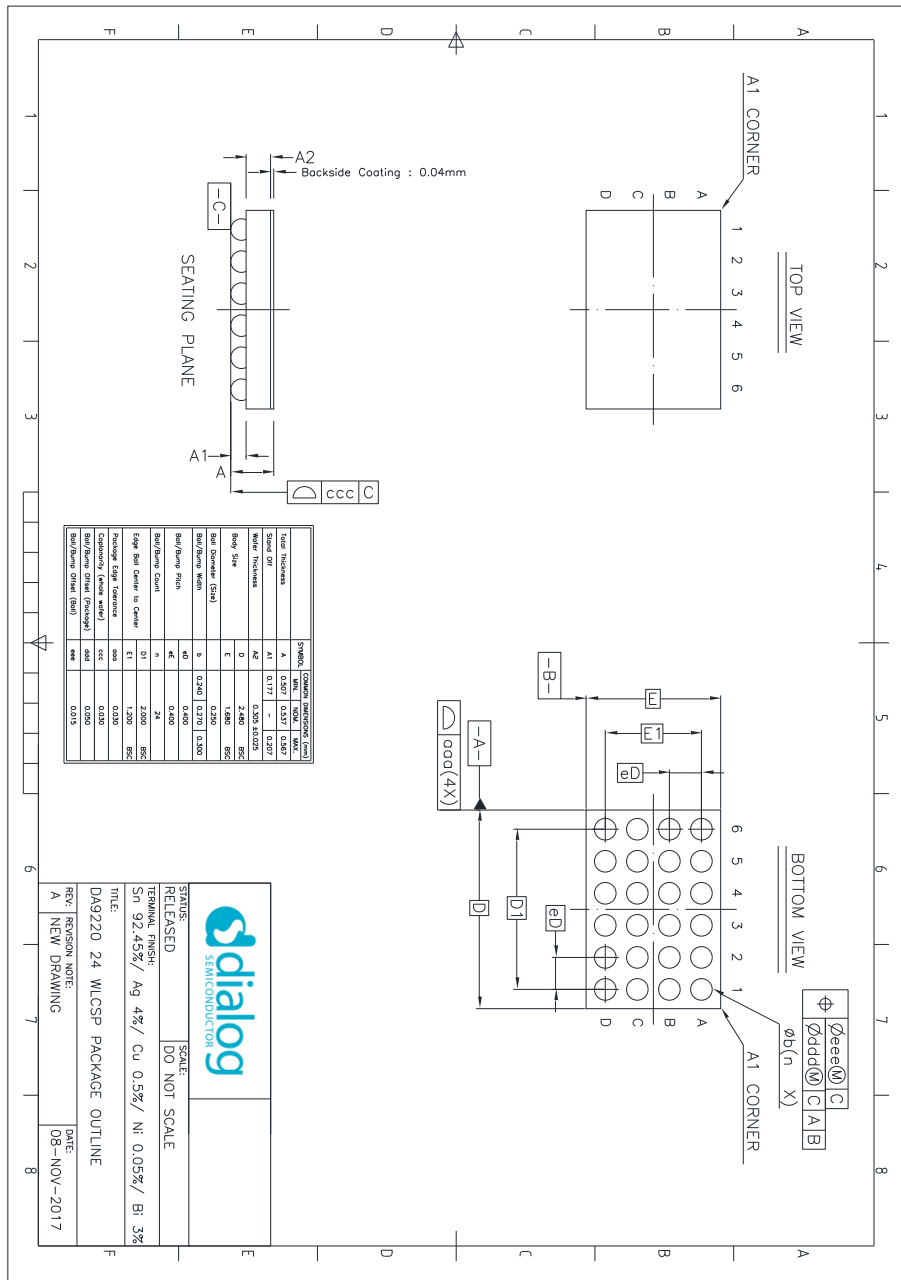


Figure 4: DA9217 and DA9220 WLCSP Package Outline Drawing

DA9217/DA9220 PCB Layout Recommendations

4.2 Buck Converter

DA9217 and DA9220 follow the standard buck layout procedure with output capacitors placed as close as possible to the load. Due to the device's ability to deliver high currents, a wide output trace for minimized parasitic impedance is recommended.

4.2.1 DA9217 and DA9220 Input

In a buck converter layout, the input capacitor location is critical. Locate the input capacitor as close as possible to the device's input and power GND pins. In DA9217 and DA9220 layout design, the input capacitor for each phase should be placed close as possible to the PVDD<x> and PGND<x> pins, and on the same layer as the DA9217 or DA9220 device. The traces between the input capacitor pads and the device's balls need to be kept as short as possible to minimize the parasitic inductance.

If multiple layers are used, it is recommended to use at least two through-hole vias (or at least six microvias) to connect the input voltage (VSYS) between layers to minimize line resistance.

The DA9217 and DA9220 have separate AVDD supply pins for the internal analog circuits. A 1 μF bypass capacitor should be placed close to the device's AVDD pin. The AVDD pin input and buck converter input (PVDD1 and PVDD2) share the same net, but it is important to separate these traces. Do not connect both traces directly on the same layer.

Ensure that the AVDD pin is connected to the input voltage (VSYS) plane far enough from the buck's input voltage plane so switching noise from the buck converter input (PVDD1 and PVDD2) is not injected to the AVDD pin.

Figure 5 shows the input capacitor placement and routing recommendation.

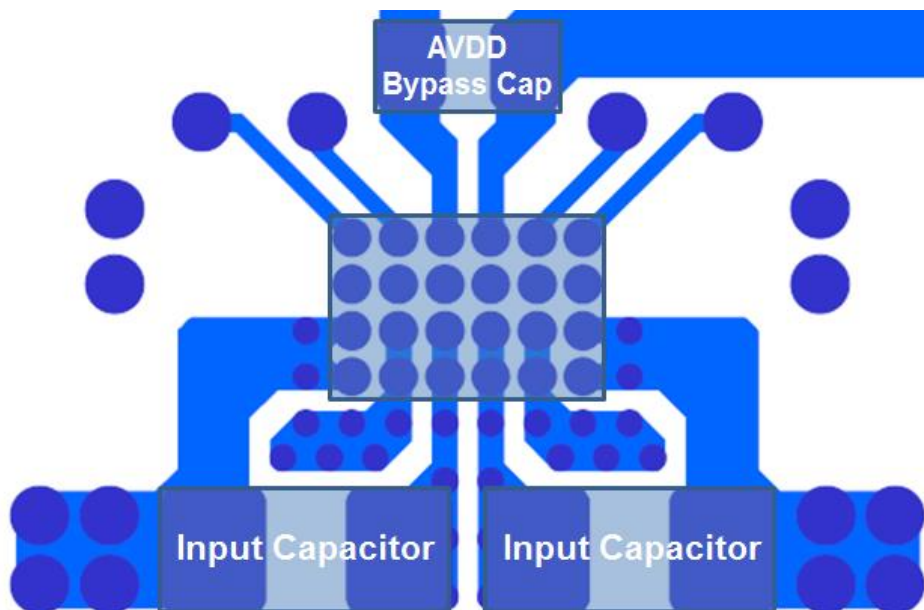


Figure 5: Recommended Input Capacitor Placement and Routing

DA9217/DA9220 PCB Layout Recommendations

4.2.2 Ground Connections

Special care should be taken with ground connections because of the high current capability of DA9217 and DA9220, and because of the device's high performance requirements.

The power GND terminals (PGND1 and PGND2) of the DA9217 and DA9220 are placed between each phase's LX pin.

For DA9220, it is strongly recommended to separate PGND1 and PGND2 on the component layer and connect them at a solid common GND plane. For DA9217, it is not necessary to separate PGND1 and PGND2.

It is best practice to isolate quiet analog GND (AGND) from noisy power GND terminals (PGND1 and PGND2) and to connect them at a single point.

Layer 2 can be used as a return power GND plane, where the device's PGND pins and output capacitor GND can be connected together. It is recommended to minimize the line impedance of the PGND pins and output capacitor GND connections by using as many vias as possible. This will also improve the heat dissipation.

NOTE

It is always recommended to use copper plugged vias to achieve the minimum parasitic via impedance and best thermal performance.

Examples of how to connect the GND terminals are illustrated in [Figure 6](#) and [Figure 7](#).

AGND is isolated from the power GND terminals (PGND1 and PGND2) at the top layer (component layer) and connected at a single point on the bottom layer.

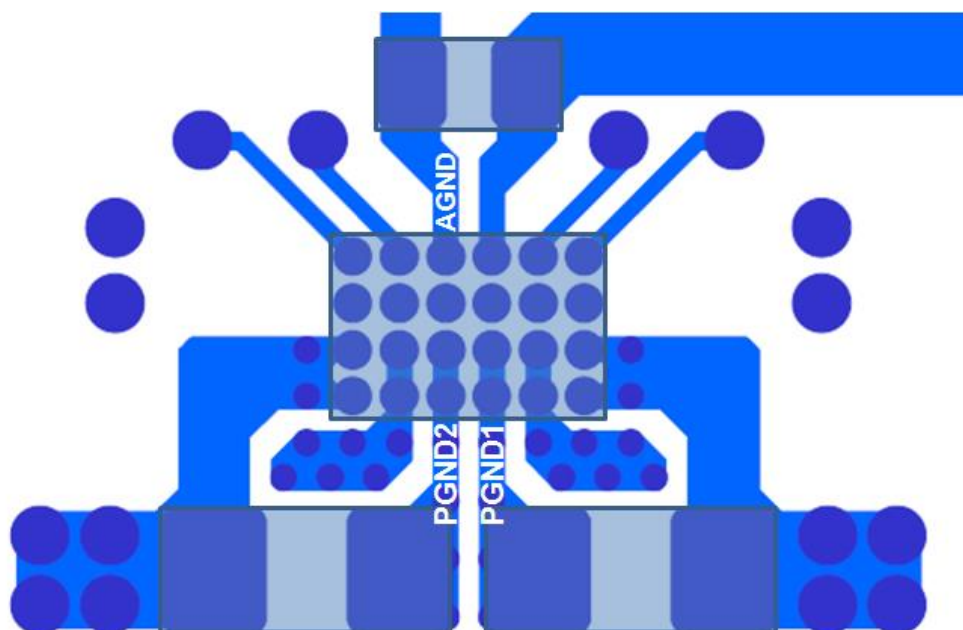


Figure 6: Recommended Grounds Connection for DA9220

DA9217/DA9220 PCB Layout Recommendations

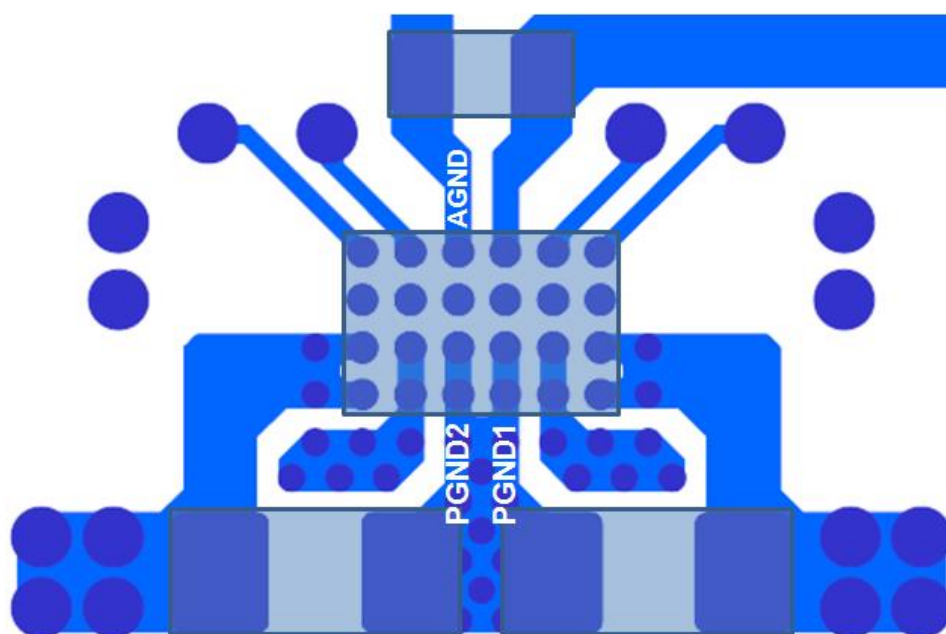


Figure 7: Recommended Grounds Connection for DA9217

4.2.3 LX Routing

Switch node/LX node traces (traces between LX pins and output inductors) need to be kept as short as possible since this node generates switching noise, which can interfere with buck converter stability. Very high current will flow through this trace and so the minimum width of trace used for this LX node must be considered. Also, ensure that there are enough vias to deliver the current.

The LX node patterns on Dialog's DA9220 Evaluation Board are shown in [Figure 8](#).

DA9217/DA9220 PCB Layout Recommendations

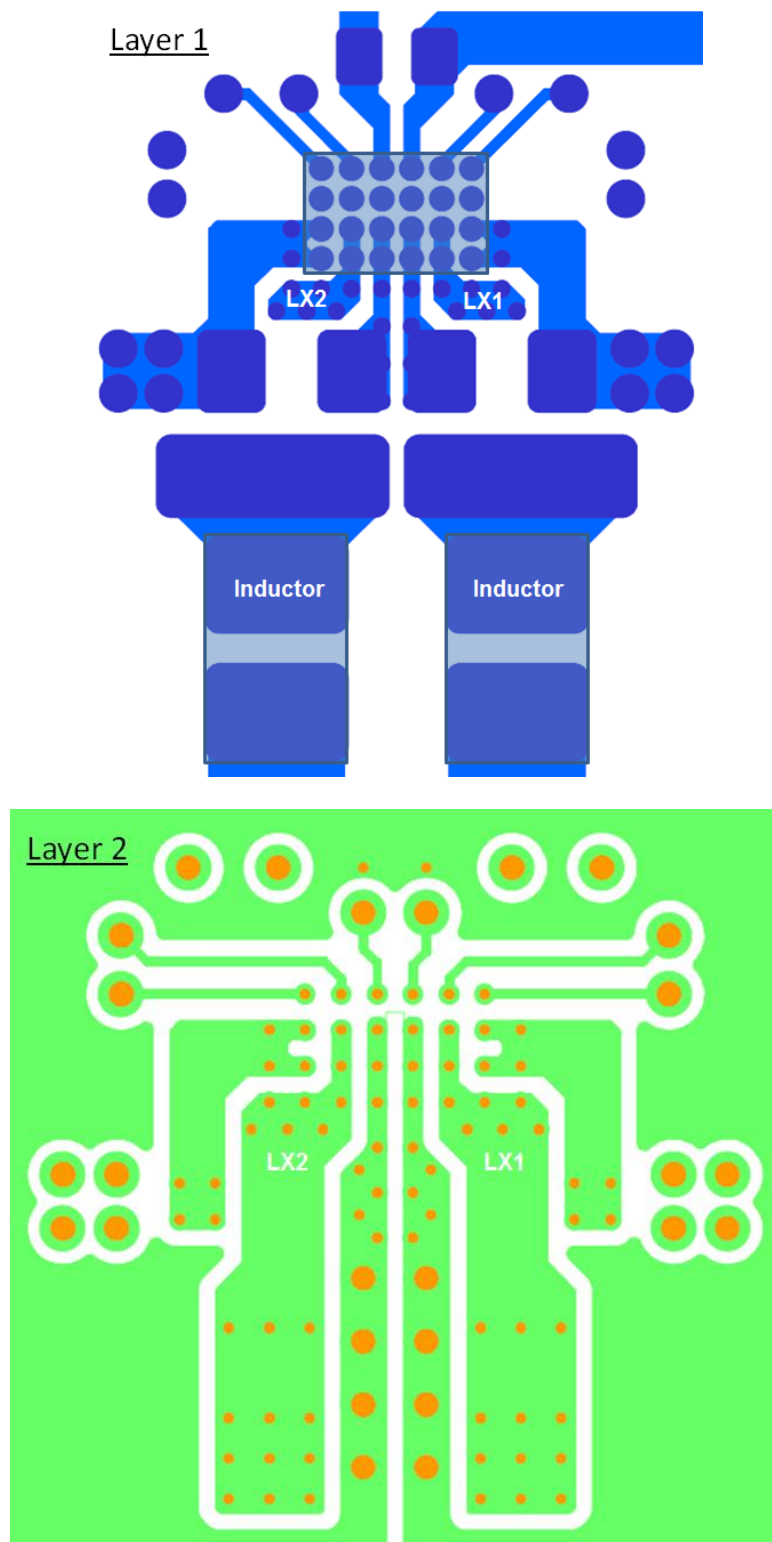


Figure 8: LX Node Pattern on DA9220 Evaluation Board

DA9217/DA9220 PCB Layout Recommendations

4.2.4 Buck Output

Output capacitors should be placed as close as possible to the load. Do not split the output capacitors into local capacitors (close to the output inductor) and remote capacitors (close to the load) as this may affect the stability of the buck converter.

However, minimizing the distance (which minimizes the line impedance) from the output inductors to the output capacitors (the load) is also important since it directly affects the efficiency and load transient response performance of the buck converter. Care must be taken with the size of the output traces since the output peak current can be up to 6 A for DA9217 and up to 3 A per-channel for DA9220.

It is best practice to transfer the output current at the top layer directly without using any vias. This will give the best performance in terms of efficiency and load transient response performance.

4.2.5 Feedback Lines

Feedback lines must be routed as a differential pair far from any noise source (for example, output inductors, LX node, and so forth). It is strongly recommended to place a bypass capacitor (typically 1 nF) between the positive and negative sides of the differential feedback. The bypass capacitor should be placed as close as possible to the IC. It is useful for filtering noise which may be injected to the feedback lines due to a layout limitation (for example, a long feedback pattern or noise from other devices in the system).

Also, ensure that the feedback lines are not overlapping any noisy node traces (for example, the LX node trace) without an insulation plane in between. Assuming that DA9217 or DA9220 is assembled on the top layer, it is recommended to route the feedback lines on Layer 4 or below when the traces are near to the IC and the switch node areas.

NOTE

- The negative feedback trace is at ground potential and care should be taken not to connect any part of the trace to the ground plane.
- The feedback lines must be routed directly from the load point in order to achieve the best voltage accuracy and stability.

Examples of output-voltage feedback-line routing, on the Dialog DA9220 Evaluation Board, are shown in [Figure 9](#).

DA9217/DA9220 PCB Layout Recommendations

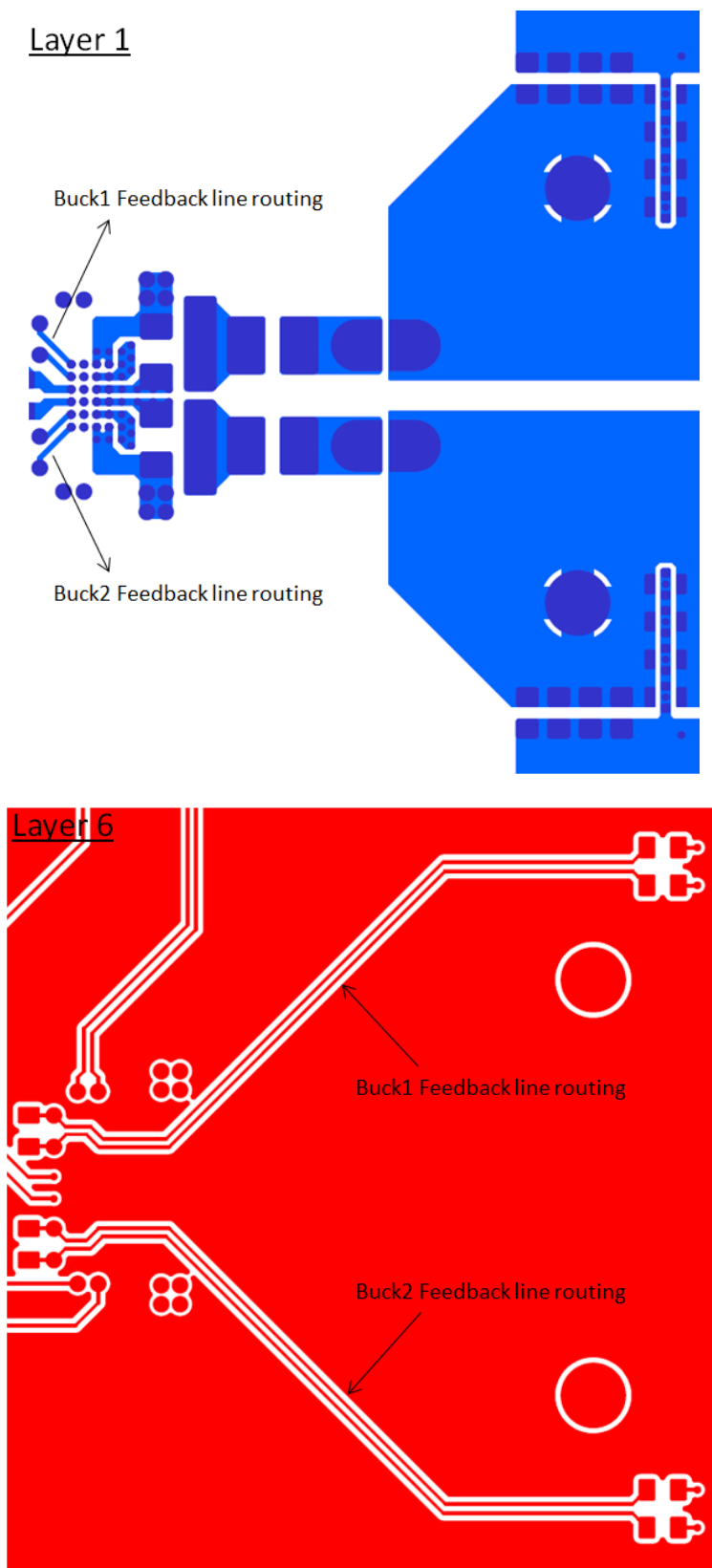


Figure 9: Output Voltage Feedback Line Routing on DA9220 Evaluation Board

DA9217/DA9220 PCB Layout Recommendations

4.3 Communication Interface (I²C)

It is recommended to route the communication interface far from any noise source.

Care must also be taken regarding the noise produced by the interface signal in order to avoid coupling to the sensitive analog references and feedbacks. The routing layer is not critical, but it is recommended to use the bottom or top layer.

4.4 GPIO Signals

Generally, GPIOs have the lowest routing priority. Any layer can be used for routing these signals.

However, care must be taken regarding the noise produced by the GPIOs in order to avoid coupling to the sensitive analog references and feedbacks.

Revision History

Revision	Date	Description
0.1	18-Jun-2018	Initial version.

DA9217/DA9220 PCB Layout Recommendations

Status Definitions

Status	Definition
DRAFT	The content of this document is under review and subject to formal approval, which may result in modifications or additions.
APPROVED or unmarked	The content of this document has been approved for publication.

Disclaimer

Information in this document is believed to be accurate and reliable. However, Dialog Semiconductor does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information. Dialog Semiconductor furthermore takes no responsibility whatsoever for the content in this document if provided by any information source outside of Dialog Semiconductor.

Dialog Semiconductor reserves the right to change without notice the information published in this document, including without limitation the specification and the design of the related semiconductor products, software and applications.

Applications, software, and semiconductor products described in this document are for illustrative purposes only. Dialog Semiconductor makes no representation or warranty that such applications, software and semiconductor products will be suitable for the specified use without further testing or modification. Unless otherwise agreed in writing, such testing or modification is the sole responsibility of the customer and Dialog Semiconductor excludes all liability in this respect.

Customer notes that nothing in this document may be construed as a license for customer to use the Dialog Semiconductor products, software and applications referred to in this document. Such license must be separately sought by customer with Dialog Semiconductor.

All use of Dialog Semiconductor products, software and applications referred to in this document are subject to Dialog Semiconductor's [Standard Terms and Conditions of Sale](#), available on the company website (www.dialog-semiconductor.com) unless otherwise stated.

Dialog and the Dialog logo are trademarks of Dialog Semiconductor plc or its subsidiaries. All other product or service names are the property of their respective owners.

© 2019 Dialog Semiconductor. All rights reserved.

Contacting Dialog Semiconductor

United Kingdom (Headquarters)

Dialog Semiconductor (UK) LTD
Phone: +44 1793 757700

Germany

Dialog Semiconductor GmbH
Phone: +49 7021 805-0

The Netherlands

Dialog Semiconductor B.V.
Phone: +31 73 640 8822

Email:

enquiry@diasemi.com

North America

Dialog Semiconductor Inc.
Phone: +1 408 845 8500

Japan

Dialog Semiconductor K. K.
Phone: +81 3 5769 5100

Taiwan

Dialog Semiconductor Taiwan
Phone: +886 281 786 222

Web site:

www.dialog-semiconductor.com

Hong Kong

Dialog Semiconductor Hong Kong
Phone: +852 2607 4271

Korea

Dialog Semiconductor Korea
Phone: +82 2 3469 8200

China (Shenzhen)

Dialog Semiconductor China
Phone: +86 755 2981 3669

China (Shanghai)

Dialog Semiconductor China
Phone: +86 21 5424 9058